

## Minterm Expression of $f(W, X, Y) = WX + XY' + WY'$

### Step 1: Truth Table

$W$	$X$	$Y$	$WX$	$XY'$	$WY'$	$f = WX + XY' + WY'$
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	1	0	1
0	1	1	0	0	0	0
1	0	0	0	0	1	1
1	0	1	0	0	0	0
1	1	0	1	1	1	1
1	1	1	1	0	0	1

### Step 2: Identify Rows Where $f = 1$

The function is true for the following combinations:

$$(0, 1, 0) \Rightarrow m_2 = W'XY'$$

$$(1, 0, 0) \Rightarrow m_4 = WX'Y'$$

$$(1, 1, 0) \Rightarrow m_6 = WXY'$$

$$(1, 1, 1) \Rightarrow m_7 = WXY$$

### Step 3: Canonical SOP (Minterm) Expression

$$f(W, X, Y) = m_2 + m_4 + m_6 + m_7$$

## Vaman Board Pin Connections

Signal	PYGMY Pins	Description
$W$	IO_28	Push button input with pull-down resistor
$X$	IO_23	Push button input with pull-down resistor
$Y$	IO_31	Push button input with pull-down resistor
$f$ (Output)	7-segment display	Active-low output to display $f$ as digit 0 or 1

*Note: Connect push buttons between input pins and 3.3V. Enable internal pull-down resistors. Use a common cathode 7-segment display. Segment logic is active-low: segment glows when output is 0.*