
Problem Setup

Given a 4:1 multiplexer:

- Select lines: a and b
- Inputs:

$$i_0 = c$$

$$i_1 = d$$

$$i_2 = \bar{c}$$

$$i_3 = \bar{c} \cdot \bar{d}$$

Step 1: MUX Output Expression

$$f(a, b, c, d) = \bar{a}\bar{b}c + \bar{a}bd + a\bar{b}\bar{c} + ab\bar{c}\bar{d}$$

Step 2: Expand Terms to Include All Variables

$$\text{Term 1: } \bar{a}\bar{b}c = \bar{a}\bar{b}c(d + \bar{d}) = \bar{a}\bar{b}cd + \bar{a}\bar{b}c\bar{d}$$

$$\text{Term 2: } \bar{a}bd = \bar{a}bd(c + \bar{c}) = \bar{a}bdc + \bar{a}bd\bar{c}$$

$$\text{Term 3: } a\bar{b}\bar{c} = a\bar{b}\bar{c}(d + \bar{d}) = a\bar{b}\bar{c}d + a\bar{b}\bar{c}\bar{d}$$

$$\text{Term 4: } ab\bar{c}\bar{d} \text{ already includes all variables}$$

Step 3: List All Resulting Minterms

Using variable order a, b, c, d (MSB to LSB):

- $\bar{a}\bar{b}cd \rightarrow 0011 = m_3$
- $\bar{a}\bar{b}c\bar{d} \rightarrow 0010 = m_2$
- $\bar{a}bdc \rightarrow 0111 = m_7$
- $\bar{a}bd\bar{c} \rightarrow 0101 = m_5$
- $a\bar{b}\bar{c}d \rightarrow 1001 = m_9$
- $a\bar{b}\bar{c}\bar{d} \rightarrow 1000 = m_8$
- $ab\bar{c}\bar{d} \rightarrow 1100 = m_{12}$

Final Answer: Sum of Minterms

$$f(a, b, c, d) = \sum m(2, 3, 5, 7, 8, 9, 12)$$

Raspberry Pi Pico Pin Connections

Signal	GPIO Pin	Purpose
<i>a</i>	GPIO 14	Select input A (push button with pull-down)
<i>b</i>	GPIO 15	Select input B (push button with pull-down)
<i>c</i>	GPIO 16	Data input (push button with pull-down)
<i>d</i>	GPIO 18	Data input (push button with pull-down)
<i>f</i>	GPIO 17	Output to LED

Note: Connect each button between the GPIO and 3.3V. Enable internal pull-down resistors. Use a current-limiting resistor with the LED from GPIO 17 to GND.